

# SerDes analog circuits description

Fávero Santos  
faverro.santos@gmail.com

Revision 00 of January 15, 2021

## Introduction

The netlists presented in this article can be seen as circuits if a netlist-to-schematic conversor (such as NetlistViewer - <https://sourceforge.net/p/netlistviewer/wiki/Home/>) is employed.



### Employed notation:

- i A DC only voltage/current is represented by an italic uppercase letter(s) followed by italic uppercase subscript letter(s).  
A DC voltage drop across the *GATE* and *SOURCE* of a transistor is represented by  $V_{GS}$ .
- ii An AC only voltage/current is represented by an italic lowercase letter(s) followed by italic lowercase subscript letter(s).  
An AC voltage drop across the *GATE* and *SOURCE* of a transistor is represented by  $v_{gs}$ .
- iii A combined DC and AC voltage/current is represented by an italic uppercase letter(s) followed by italic lowercase subscript letter(s).  
A combined DC and AC voltage drop across the *GATE* and *SOURCE* of a transistor is represented by  $V_{gs}$ .

An example of such notation is presented in Figure 1.

## 1 Analysis of an RC channel

### 1.1 Transfer function

Consider the circuit

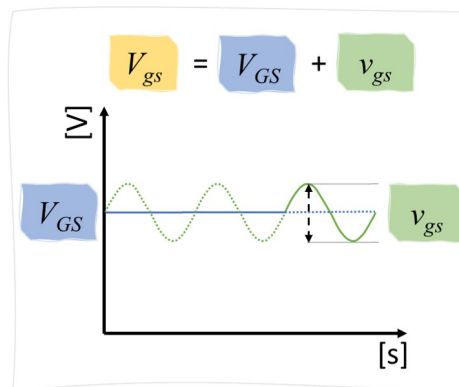


Figure 1: Examples of the employed notation in this work.

*Netlist of an RC circuit*

```
.SUBCKT RCchannel vin vout  
R1 vin vout R  
C1 vout gnd! C  
.ENDS
```

At node vout(s):

$$v_{out}(s) = i(s) \cdot 1/(s \cdot C)$$

$$v_{in}(s) - v_{out}(s) = i(s) \cdot R$$

$$v_{in}(s) - i(s) \cdot 1/(s \cdot C) = i(s) \cdot R$$

$$v_{in}(s) = i(s) \cdot (R + 1/(s \cdot C))$$

Thus

$$\frac{v_{out}(s)}{v_{in}(s)} = H(s) = \frac{i(s) \cdot 1/(s \cdot C)}{i(s) \cdot (R + 1/(s \cdot C))}$$

*Transfer function for an RC circuit*

$$H(s) = \frac{\omega_a}{s + \omega_a}$$

Where  $\tau = R \cdot C$  and  $\omega_a = 1/\tau$ .

## 1.2 Impulse response

Applying the inverse Laplace transform in the transfer function, it is obtained:

*Impulse response for an RC circuit*

$$h(t) = \omega_a \cdot \exp(-t \cdot \omega_a)$$

for  $t > 0$ .

## 1.3 Magnitude of the transfer function

$$|H(s)| = \left| \frac{\omega_a}{s + \omega_a} \right|$$

*Magnitude of  $H(s)$*

$$|H(s)| = \frac{\omega_a}{\sqrt{w^2 + \omega_a^2}}$$

## 1.4 Phase of the transfer function

$$\theta(w) = \arctan\left(\frac{\Im H(w)}{\Re H(w)}\right)$$

$$H(w) = \frac{\omega_a}{i \cdot w + \omega_a} = \frac{\omega_a \cdot (-i \cdot w + \omega_a)}{(i \cdot w + \omega_a) \cdot (-i \cdot w + \omega_a)}$$

$$H(w) = \frac{\omega_a^2 - i \cdot \omega \cdot \omega_a}{\omega^2 + \omega_a^2}$$

$$\Re H(w) = \frac{\omega_a^2}{\omega^2 + \omega_a^2}$$

$$\Im H(w) = \frac{-\omega \cdot \omega_a}{\omega^2 + \omega_a^2}$$

*Phase of  $H(w)$*

$$\theta(w) = \arctan(-\omega/\omega_a)$$

## 1.5 Quantization of the model

Considering that  $\omega_a = \omega_d/FS$ , where FS is the sampling frequency, the quantized model is:

*Transfer function for an RC circuit*

$$H[m] = \frac{\omega_d/FS}{s + \omega_d/FS}$$

Where m is a discrete frequency vector.

*Impulse response for an RC circuit*

$$h[n] = (\omega_d/FS) \cdot \exp(-n \cdot (\omega_d/FS))$$

Where n is a discrete time vector.

*Magnitude of  $H(w)$*

$$|H[m]| = \frac{\omega_d/FS}{\sqrt{\omega^2 + (\omega_d/FS)^2}}$$

*Phase of  $H(w)$*

$$\theta[m] = \arctan(-\omega/(\omega_d/FS))$$

## 2 Analysis of a constant time linear equalizer

### 2.1 Transfer function

Consider the circuit

#### Netlist of a CTLE

```
.SUBCKT CTLE vinp vinn voutp voutn gnd!  
R1 gnd! voutp RD  
M1 voutp vinp vs1 0 M1  
I1 vs1 gnd! I1  
R2 gnd! voutn RD  
M2 voutn vinn vs2 0 M2  
I2 vs2 gnd! I2  
R3 vs1 vs2 RS  
C1 vs1 vs2 CS  
.ENDS
```

Its transfer function is:

Transfer function for a CTLE circuit

$$H(s) = \frac{-g_m \cdot R_D \cdot (s + \omega_a)}{(s + \omega_a \cdot (\tau + h))}$$

Where  $\tau = RS \cdot CS$ ,  $\omega_a = 1/\tau$ , and  $h = g_m \cdot RS/2$ .

## 2.2 Impulse response

Transfer function for a CTLE circuit

$$h(t) = -g_m \cdot R_D \cdot \omega_a \cdot (1 - h - \tau) \cdot \exp(-t \cdot \omega_a \cdot (h + \tau))$$

For  $t > 0$ .

## 2.3 Magnitude of the transfer function

$$|H(w)| = \frac{g_m \cdot R_D \cdot \sqrt{\omega_a^2 + w^2}}{\sqrt{(\omega_a \cdot (\tau + h))^2 + w^2}}$$

## 2.4 Phase of the transfer function

$$\Re H(w) = \frac{g_m \cdot R_D \cdot (\omega^2 + \omega_a^2 \cdot (\tau + h))}{\omega^2 + \omega_a^2 \cdot (\tau + h)^2}$$

$$\Im H(w) = \frac{g_m \cdot R_D \cdot \omega \cdot \omega_a \cdot (\tau + h - 1)}{\omega^2 + \omega_a^2 \cdot (\tau + h)^2}$$

Phase of  $H(w)$

$$\theta(w) = \arctan \frac{\omega \cdot \omega_a \cdot (\tau + h - 1)}{\omega^2 + \omega_a^2 \cdot (\tau + h)^2}$$

## 2.5 Quantization of the model

Considering that  $\omega_a = \omega_a/FS$ , where FS is the sampling frequency, the quantized model is:

Transfer function for a CTLE circuit

$$H[m] = \frac{-g_m \cdot R_D \cdot (s + (\omega_d / FS))}{(s + (\omega_d / FS) \cdot (\tau + h))}$$

Transfer function for a CTLE circuit

$$h[n] = -g_m \cdot R_D \cdot (\omega_d / FS) \cdot (1 - h - \tau) \cdot \exp(-n \cdot (\omega_d / FS) \cdot (h + \tau))$$

Magnitude of  $H(w)$

$$|H[m]| = \frac{g_m \cdot R_D \cdot \sqrt{(\omega_d / FS)^2 + \omega^2}}{\sqrt{((\omega_d / FS) \cdot (\tau + h))^2 + \omega^2}}$$

Phase of  $H(w)$

$$\theta[m] = \arctan \frac{\omega \cdot (\omega_d / FS) \cdot (\tau + h - 1)}{\omega^2 + (\omega_d / FS)^2 \cdot (\tau + h)^2}$$

### 3 Example code

An example code for such study can be found at: <https://github.com/faverosantos/SerDes>

### References