

SerDes analog circuits description

Fávero Santos
faverro.santos@gmail.com

Revision 00 of January 14, 2021

1 Introduction

①

Employed notation:

- i A DC only voltage/current is represented by an italic uppercase letter(s) followed by italic uppercase subscript letter(s).

A DC voltage drop across the *GATE* and *SOURCE* of a transistor is represented by V_{GS} .

- ii An AC only voltage/current is represented by an italic lowercase letter(s) followed by italic lowercase subscript letter(s).

An AC voltage drop across the *GATE* and *SOURCE* of a transistor is represented by v_{gs} .

- iii A combined DC and AC voltage/current is represented by an italic uppercase letter(s) followed by italic lowercase subscript letter(s).

A combined DC and AC voltage drop across the *GATE* and *SOURCE* of a transistor is represented by V_{gs} .

An example of such notation is presented in Figure 1.

Analysis of an RC channel

1.1 Transfer function

Consider the circuit

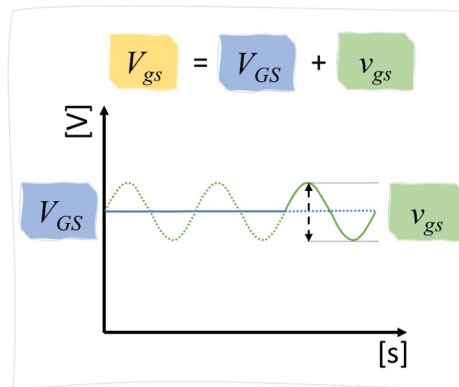


Figure 1: Examples of the employed notation in this work.

①

Netlist in terms of time of an RC circuit

```
R1 vin(t) vout(t) R
C1 vout(t) gnd!(t) C
```

in which the a current $i(t)$ is sourced in the $vin(t)$ node and drained at $gnd!$
Applying the Laplace transform, the circuit becomes

①

Netlist in terms of frequency of an RC circuit

```
R1 vin(s) vout(s) R
C1 vout(s) gnd!(t) 1/sC
```

At node $vout(s)$:

$$v_{out}(s) = i(s) \cdot 1/(s \cdot C)$$

$$v_{in}(s) - v_{out}(s) = i(s) \cdot R$$

$$v_{in}(s) - i(s) \cdot 1/(s \cdot C) = i(s) \cdot R$$

$$v_{in}(s) = i(s) \cdot (R + 1/(s \cdot C))$$

Thus

$$\frac{v_{out}(s)}{v_{in}(s)} = H(s) = \frac{i(s) \cdot 1/(s \cdot C)}{i(s) \cdot (R + 1/(s \cdot C))}$$

Transfer function for an RC circuit

$$H(s) = \frac{\omega_a}{s + \omega_a}$$

Where $\tau = R \cdot C$ and $\omega_a = 1/\tau$.

1.2 Impulse response

Applying the inverse Laplace transform in the transfer function, it is obtained:

Impulse response for an RC circuit

$$h(t) = \omega_a \cdot \exp(-t \cdot \omega_a)$$

for $t > 0$.

1.3 Magnitude of the transfer function

$$|H(s)| = \left| \frac{\omega_a}{s + \omega_a} \right|$$

Magnitude of $H(s)$

$$|H(s)| = \frac{\omega_a}{\sqrt{\omega^2 + \omega_a^2}}$$

1.4 Phase of the transfer function

$$\theta(s) = \arctan\left(\frac{\Im H(s)}{\Re H(s)}\right)$$

$$H(s) = \frac{\omega_a}{i\omega + \omega_a} = \frac{\omega_a \cdot (-i\omega + \omega_a)}{(i\omega + \omega_a) \cdot (-i\omega + \omega_a)}$$

$$H(s) = \frac{\omega_a^2 - i\omega \cdot \omega_a}{\omega^2 + \omega_a^2}$$

$$\Re H(s) = \frac{\omega_a^2}{\omega^2 + \omega_a^2}$$

$$\Im H(s) = \frac{-\omega \cdot \omega_a}{\omega^2 + \omega_a^2}$$

Phase of $H(s)$

$$\theta(s) = \arctan(-\omega/\omega_a)$$

1.5 Quantization of the model

Considering that $\omega_a = \omega_d/FS$, where FS is the sampling frequency, the quantized model is:

Transfer function for an RC circuit

$$H[m] = \frac{\omega_d/FS}{s + \omega_d/FS}$$

Where m is a discrete frequency vector.

Impulse response for an RC circuit

$$h[n] = (\omega_d/FS) \cdot \exp(-t * \omega_d/FS)$$

Where n is a discrete time vector.

Magnitude of $H(s)$

$$|H[m]| = \frac{\omega_d/FS}{\sqrt{\omega^2 + \omega_d^2/FS^2}}$$

Phase of $H(s)$

$$\theta(s) = \arctan(-\omega/\omega_d/FS)$$

2 Example code

An example code for such study can be found at: <https://github.com/faverosantos/SerDes>

References